

## Set3



ECE 390: WORKSHOP ON ANALOG DESIGN USING CADENCE  
VIRTUOSO


Name: Mohit Rawat


Section: E1901 Roll No: 09

Registration No: 11904463

Max Marks: 30

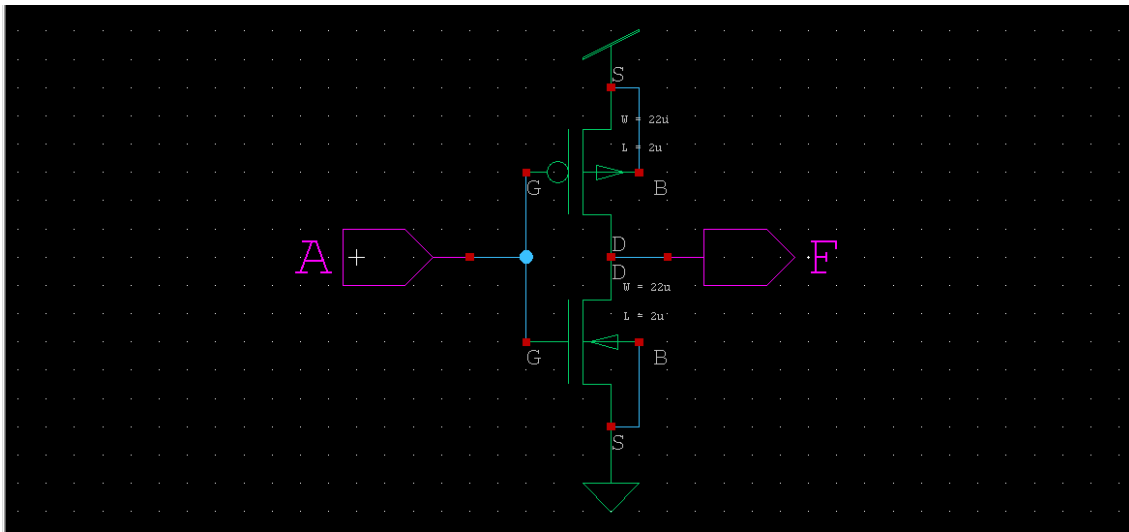
Q1. Design a CMOS inverter using tanner tool and create a symbol named NOT gate of the same.



 

5)

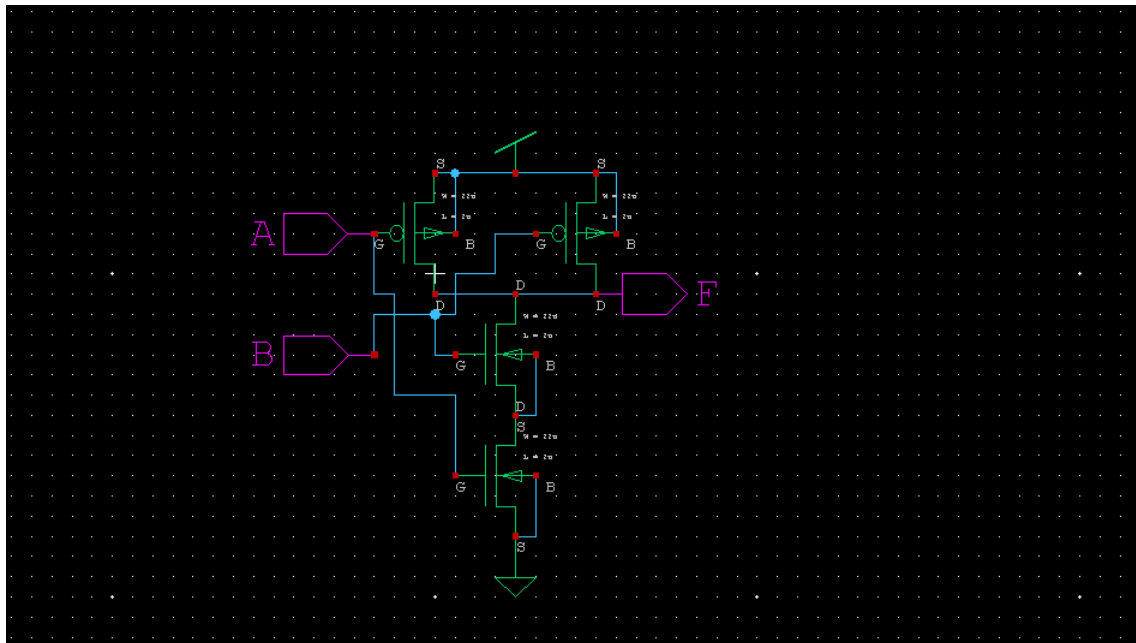Q2. Implement NAND gate using CMOS technology and simulate on tanner tool using level 1 model file. Attach the screenshots of S-edit, T-spice and W-Edit of the same.




```

***** Simulation Settings - Parameters and SPICE Options *****
MMOSFET_N_1 F B N_1 N_1 NMOS L=2u W=22u AD=66p PD=24u AS=66p PS=24u
MMOSFET_N_2 N_1 A Gnd Gnd NMOS L=2u W=22u AD=66p PD=24u AS=66p PS=24u
MMOSFET_P_2 F A Vdd Vdd PMOS L=2u W=22u AD=66p PD=24u AS=66p PS=24u
MMOSFET_P_3 F B Vdd Vdd PMOS L=2u W=22u AD=66p PD=24u AS=66p PS=24u

***** Simulation Settings - Analysis section *****
.Model NMOS NMOS (Vto=0.8V Kp=45u Lambda=0.01 Gamma=0.4 phi=0.6)
.Model PMOS PMOS (Vto=-0.9V Kp=33u Lambda=0.02 Gamma=0.4 phi=0.6)


Vdd Vdd Gnd 3.3V
Vin1 A Gnd pulse(0 3.3v 40n 1n 1n 40n 40n)
Vin2 B Gnd pulse(0 3.3v 20n 1n 1n 20n 40n)
.Tran 1ns 80ns
.print V(A) V(B) V(F)
***** Simulation Settings - Additional SPICE commands *****
.end



```

 


(5)

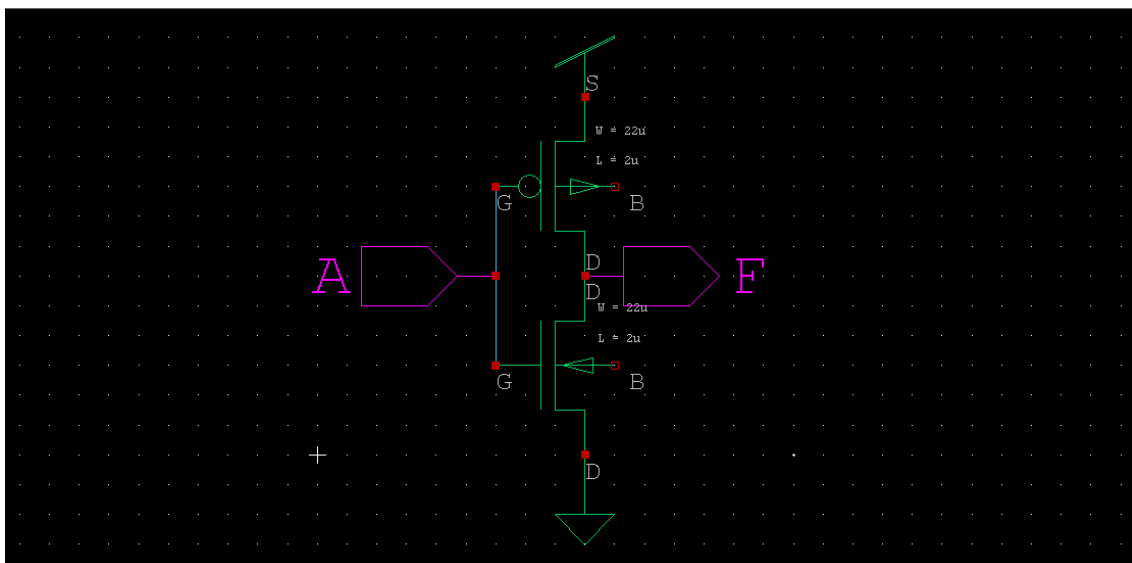Q3. Design CMOS inverter in S-edit, simulate for transient analysis in T-spice. Calculate propagation delay using the generated waveform.



  



 


```

***** Simulation Settings - Analysis section *****
.Model NMOS NMOS (Vto=0.8V Kp=45u Lambda=0.01 Gamma=0.4 phi=0.6)
.Model PMOS PMOS (Vto=-0.9V Kp=33u Lambda=0.02 Gamma=0.4 phi=0.6)


Vdd Vdd Gnd 3.3V
Vin1 A Gnd pulse(0 3.3v 40n 1n 1n 40n 40n)
Vin2 B Gnd pulse(0 3.3v 20n 1n 1n 20n 40n)
Vin3 Cin Gnd pulse(0 3.3v 10n 1n 1n 10n 20n)
.Tran 1ns 80ns
.print V(A) V(B) V(Cin) V(Sum) V(Carry)
***** Simulation Settings - Additional SPICE commands *****

.end


```


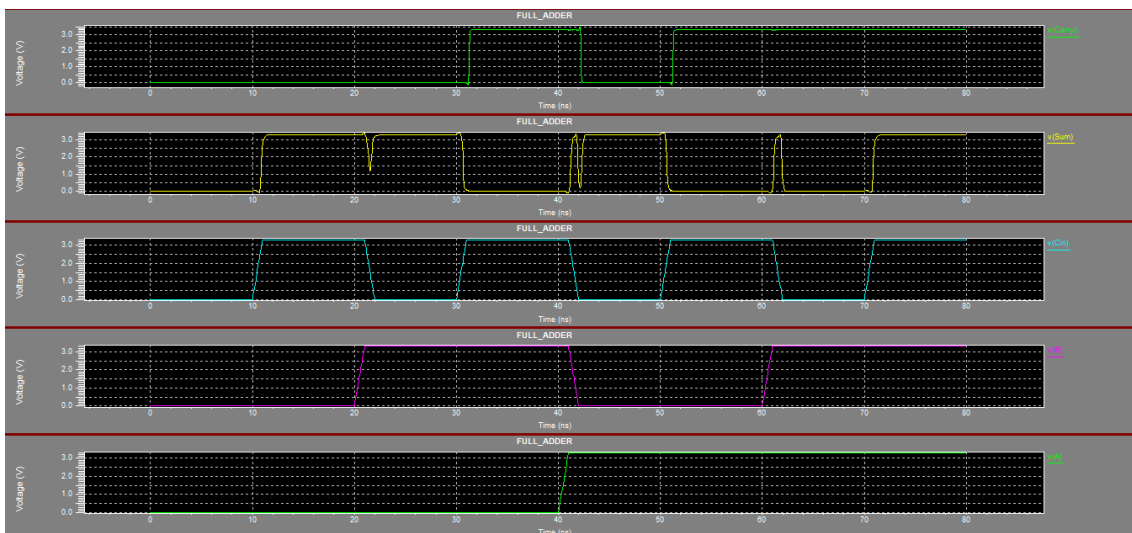


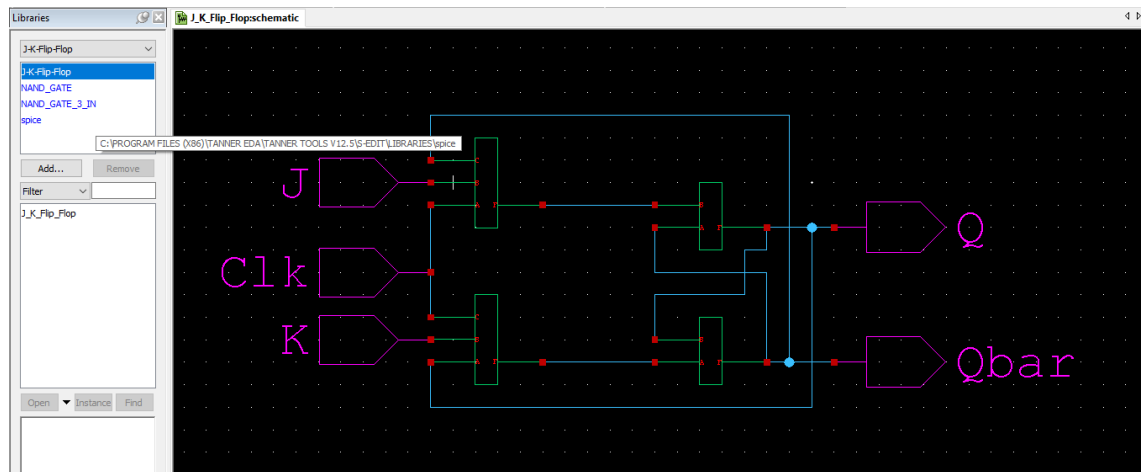Q5. Design J-K flip-flop in S-edit using instances of earlier designed NAND and Not gates as symbols, simulate for transient analysis in T-spice. Calculate propagation delay using the generated waveform.




(5)

 

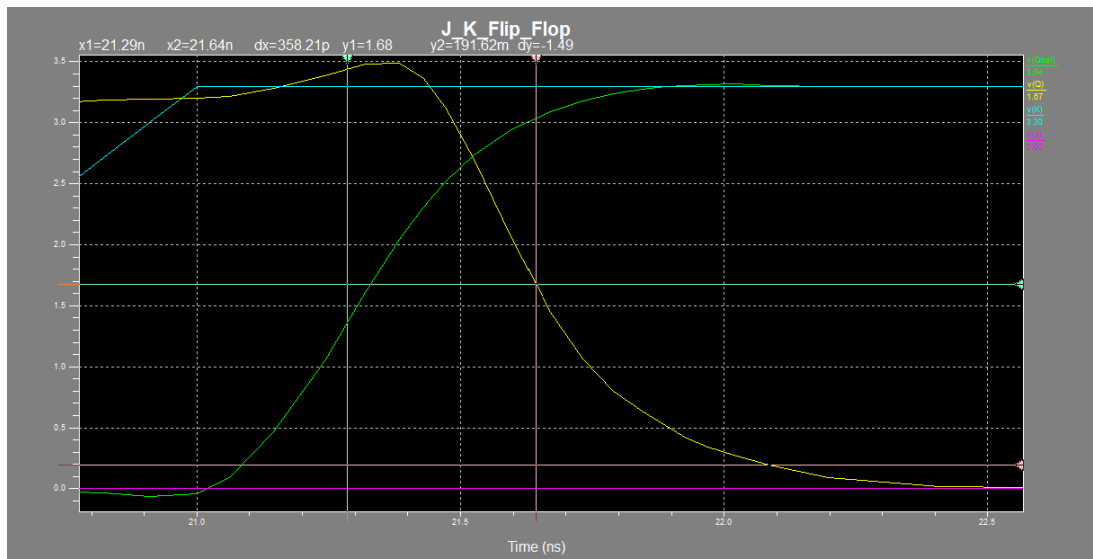 



 Q6. Design 4 bit Shift register using D flip-flop in S-edit, simulate for transient analysis in Tspice. Verify the functionality by giving input pattern 1101 in serial fashion.



```


XD_Flip_Flop_1 Clk In N_1 N_2 Gnd Vdd D_Flip_Flop
XD_Flip_Flop_2 Clk N_1 N_3 N_4 Gnd Vdd D_Flip_Flop
XD_Flip_Flop_3 Clk N_3 N_5 N_6 Gnd Vdd D_Flip_Flop
XD_Flip_Flop_4 Clk N_5 Out N_7 Gnd Vdd D_Flip_Flop

***** Simulation Settings - Analysis section *****
.Model NMOS NMOS (Vto=0.8V Kp=45u Lambda=0.01 Gamma=0.4 phi=0.6)
.Model PMOS PMOS (Vto=-0.9V Kp=33u Lambda=0.02 Gamma=0.4 phi=0.6)

Vdd Vdd Gnd 3.3V
Vin1 In Gnd pulse(0 3.3v 0 1n 1n 40n 60n)
Vin2 Clk Gnd pulse(0 3.3v 0 1n 1n 10n 20n)
.Tran 1ns 80ns
.print V(In) V(Clk) V(Out)
***** Simulation Settings - Additional SPICE commands *
*****

.end

```

 

(5)